

EEE/CSE 120

Capstone Design Project

Name: El Hadji Bane

Instructor: Doctor Steve

Class Time: @ 10:30 Tuesday & Thursday

Date: 4/21/2024

Task C-1: Planning the Synchronous Sequential Machines

(5 pts) Interview at least 3 stakeholders, but 3 is preferred. Ask questions regarding the form, function, and features needed by potential customers for this design. Make sure to capture what the customer prefers from this type of solution, as well as what environment the customer plans to use this design. Summarize your findings here and document the names of who you interviewed.

1) Questions

- a) When the capstone key fob's button is pressed while distant from your car, what do you expect the car to do?
- b) Would you rather have the key fob button presses override the auto-locking system or have the auto-locking system override the button presses.
- c) When the button is held for multiple clock cycles, what do you expect the car to do?

2) Answers

a) Annelise

- i) beep and stay locked and not flashlights.
- ii) button press override auto-locking.
- iii) continue to beep or flash until not holding.

b) Siri

- i) Do nothing when far.
- ii) Key fob over auto-locking.
- iii) Watch for pressing and release to continue normal functioning.

c) Aryan

- i) Will lock.
- ii) Button over auto.
- iii) The state should be maintained.

d) Steve

- i) do nothing.
- ii) auto over button.
- iii) register as a single button press.

3) Findings:

- a) When distant, the fob should be locked regardless of the button presses.

Commented [A1]: findings

- b) The button presses should override the auto-locking system.
- c) Holding down the button and releasing should register as a single press.

(5 pts) Please include a comment on why your automation adds value from multiple perspectives (technological, societal, financial, environmental, etc.). (What value does this add? What is the type of customer for whom this is designed? Where is this most needed? What couldn't you do before?)

The larger the sample group, the better insight I have on what a general audience would want for the auto-locking key fob. Getting multiple perspectives also helps me incorporate features and safeguards I wouldn't have considered initially.

(5 pts) It is allowable to continue to ask questions of stakeholders throughout the design process (and is preferred of a conscientious engineer). This can be done as you are designing, before you are designing if you need input and clarifications, or after you are done designing if you want feedback on improvements. Summarize any changes to your understanding or design based on the feedback you received during your initial interviews or continual interviews?

- The stakeholders don't want the car to be unlockable when they press the button.
- The stakeholders want control over the auto-locking.
- The stakeholders consider the press and release as 1 button press.

Task C-2: Document the Synchronous Sequential Machines

Design #1: (2 pts) What assumptions did you make in the design of this machine?


- The car can be unlocked regardless of the distance.
- Button presses are prioritized over the auto-locking.
- The car locks on reset.

(3 pts) Create a state definition table here that describes in plain English what each state in your machine means and what binary values you have assigned to represent each state, inputs, and outputs.


State	Name	Definition	Binary
S0	Wait	Keeps the car unlocked while watching for auto-locking conditions.	000
S1	Locking	Locks and honks the car when the car is initially locked.	001
S2	Locked	Keeps the car locked.	010
S3	Unlocking	unlocks and flashes the car when the car is initially unlocked.	011
S4	Unlocked	Keeps the car unlocked.	100


(12 pts) Show your state diagrams, state transition tables and your circuit planning work (Karnaugh maps/equations/MUX/DEC/etc.) used in your design process. (You can do this by hand if you wish, do

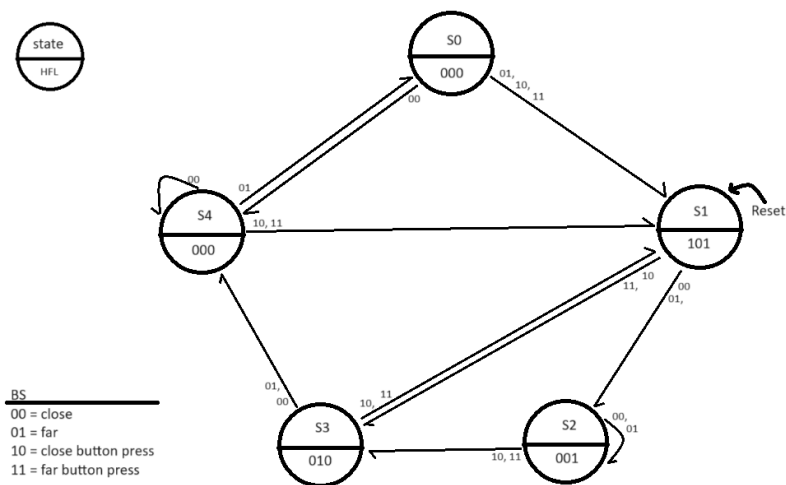not show the full circuit schematic here.)



	A	B	C	D	E	F	G	H	I	J	K	L
1	Current			Input		Future			Output			
2	State	Q0	Q1	Q2	B	S	Q0+	Q1+	Q2+	H	F	L
3	S0	0	0	0	0	0	1	0	0	0	0	0
4	S0	0	0	0	0	1	0	0	1	0	0	0
5	S0	0	0	0	1	0	0	0	1	0	0	0
6	S0	0	0	0	1	1	0	0	1	0	0	0
7	S1	0	0	1	0	0	0	1	0	1	0	1
8	S1	0	0	1	0	1	0	1	0	1	0	1
9	S1	0	0	1	1	0	0	1	1	1	0	1
10	S1	0	0	1	1	1	0	1	1	1	0	1
11	S2	0	1	0	0	0	0	1	0	0	0	1
12	S2	0	1	0	0	1	0	1	0	0	0	1
13	S2	0	1	0	1	0	0	1	1	0	0	1
14	S2	0	1	0	1	1	0	1	1	0	0	1
15	S3	0	1	1	0	0	1	0	0	0	1	0
16	S3	0	1	1	0	1	1	0	0	0	1	0
17	S3	0	1	1	1	0	0	0	1	0	1	0
18	S3	0	1	1	1	1	0	0	1	0	1	0
19	S4	1	0	0	0	0	1	0	0	0	0	0
20	S4	1	0	0	0	1	0	0	0	0	0	0
21	S4	1	0	0	1	0	0	0	1	0	0	0
22	S4	1	0	0	1	1	0	0	1	0	0	0
23	S5	1	0	1	X	X	X	X	X	X	X	X
24	S5	1	0	1	X	X	X	X	X	X	X	X
25	S5	1	0	1	X	X	X	X	X	X	X	X
26	S5	1	0	1	X	X	X	X	X	X	X	X
27	S6	1	1	0	X	X	X	X	X	X	X	X
28	S6	1	1	0	X	X	X	X	X	X	X	X
29	S6	1	1	0	X	X	X	X	X	X	X	X
30	S6	1	1	0	X	X	X	X	X	X	X	X
31	S7	1	1	1	X	X	X	X	X	X	X	X
32	S7	1	1	1	X	X	X	X	X	X	X	X
33	S7	1	1	1	X	X	X	X	X	X	X	X
34	S7	1	1	1	X	X	X	X	X	X	X	X

Single table implicant = 

Multi table implicant = 

		Q0' Q2+				Q0 Q2+			
Q1Q2	B S	00	01	11	10	00	01	11	10
00							X	X	X
01		1					X	X	X
11		1	1	1	1	1	X	X	X
10		1	1	1	1	1	X	X	X

		Q0' Q1+				Q0 Q1+			
Q1Q2	B S	00	01	11	10	00	01	11	10
00			1		1		X	X	X
01			1		1		X	X	X
11			1		1		X	X	X
10			1		1		X	X	X

	Q0' Q0+				Q0 Q0+			
Q1Q2 B S	00	01	11	10	00	01	11	10
00	1		1		1	X	X	X
01			1			X	X	X
11						X	X	X
10						X	X	X

	Q0' H				Q0 H			
Q1Q2 B S	00	01	11	10	00	01	11	10
00		1				X	X	X
01		1				X	X	X
11		1				X	X	X
10		1				X	X	X

	Q0' F				Q0 F			
Q1Q2 B S	00	01	11	10	00	01	11	10
00			1			X	X	X
01			1			X	X	X
11			1			X	X	X
10			1			X	X	X

	Q0' L				Q0 L			
Q1Q2 B S	00	01	11	10	00	01	11	10
00		1		1		X	X	X
01		1		1		X	X	X
11		1		1		X	X	X
10		1		1		X	X	X

(3 pts) List your final design equations and required logic gates (including types of Flip Flops) needed to complete this circuit.

- Equations
 - $Q_2^+ = B + Q_0'Q_1'Q_2'S$
 - $Q_1^+ = Q_1 \oplus Q_2$
 - $Q_0^+ = Q_1'Q_2'B'S' + Q_1Q_2B'$
 - $H = Q_1'Q_2$
 - $F = Q_1Q_2$
 - $L = Q_1 \oplus Q_2$
- Logic gates
 - XOR * 1 (XOR $Q_1 \oplus Q_2$ pair is repeated, so only one pair will be used in circuit)
 - AND * 5
 - OR * 2
 - D-FLIP FLOP, ASYNCHRONOUS * 3


Design #2: (2 pts) What assumptions did you make in the design of this machine?

- Holding the button down keeps the car at a state.
- The button press can override the wait.
- The car locks on reset.


(3 pts) Create a state definition table here that describes in plain English what each state in your machine means and what binary values you have assigned to represent each state.


State	Name	Definition	Binary
S0	Wait	Keeps the car unlocked while watching for auto-locking conditions.	000
S1	Locking	Locks and honks the car when the car is initially locked.	001
S2	Locked	Keeps the car locked.	010
S3	Unlocking	unlocks and flashes the car when the car is initially unlocked.	011
S4	Unlocked	Keeps the car unlocked.	100

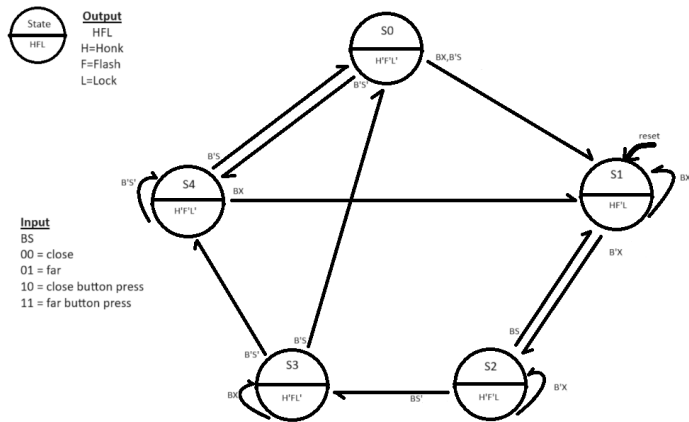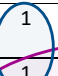
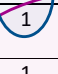

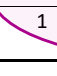
(12 pts) Show your state diagrams, state transition tables and your circuit planning work (Karnaugh maps/equations/MUX/DEC/etc.) used in your design process. (You can do this by hand if you wish, do not show the full circuit schematic here.)

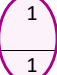
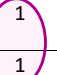

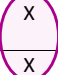





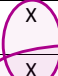






	A	B	C	D	E	F	G	H	I	J	K	L
1	Current			Input		Future			Output			
2	State	Q0	Q1	Q2	B	S	Q0+	Q1+	Q2+	H	F	L
3	S0	0	0	0	0	0	1	0	0	0	0	0
4	S0	0	0	0	0	1	0	0	1	0	0	0
5	S0	0	0	0	1	0	0	0	1	0	0	0
6	S0	0	0	0	1	1	0	0	1	0	0	0
7	S1	0	0	1	0	0	0	1	0	1	0	1
8	S1	0	0	1	0	1	0	1	0	1	0	1
9	S1	0	0	1	1	0	0	0	1	1	0	1
10	S1	0	0	1	1	1	0	0	1	1	0	1
11	S2	0	1	0	0	0	0	1	0	0	0	1
12	S2	0	1	0	0	1	0	1	0	0	0	1
13	S2	0	1	0	1	0	0	1	1	0	0	1
14	S2	0	1	0	1	1	0	0	1	0	0	1
15	S3	0	1	1	0	0	1	0	0	0	1	0
16	S3	0	1	1	0	1	0	0	0	0	1	0
17	S3	0	1	1	1	0	0	1	1	0	1	0
18	S3	0	1	1	1	1	0	1	1	0	1	0
19	S4	1	0	0	0	0	1	0	0	0	0	0
20	S4	1	0	0	0	1	0	0	0	0	0	0
21	S4	1	0	0	1	0	0	0	1	0	0	0
22	S4	1	0	0	1	1	0	0	1	0	0	0
23	S5	1	0	1	X	X	X	X	X	X	X	X
24	S5	1	0	1	X	X	X	X	X	X	X	X
25	S5	1	0	1	X	X	X	X	X	X	X	X
26	S5	1	0	1	X	X	X	X	X	X	X	X
27	S6	1	1	0	X	X	X	X	X	X	X	X
28	S6	1	1	0	X	X	X	X	X	X	X	X
29	S6	1	1	0	X	X	X	X	X	X	X	X
30	S6	1	1	0	X	X	X	X	X	X	X	X
31	S7	1	1	1	X	X	X	X	X	X	X	X
32	S7	1	1	1	X	X	X	X	X	X	X	X
33	S7	1	1	1	X	X	X	X	X	X	X	X
34	S7	1	1	1	X	X	X	X	X	X	X	X

Single table implicant = 

Multi table implicant = 

		Q0' Q2+				Q0 Q2+			
Q1Q2 B S		00	01	11	10	00	01	11	10
00							X	X	X
01							X	X	X
11			1	1	1		X	X	X
10		1	1	1	1		X	X	X

		Q0' Q1+				Q0 Q1+			
Q1Q2 B S		00	01	11	10	00	01	11	10
00								X	
01								X	
11							X		X
10							X		

	Q0' Q0+				Q0 Q0+			
Q1Q2 B S	00	01	11	10	00	01	11	10
00	1		1		1	X	X	X
01						X	X	X
11						X	X	X
10						X	X	X

	Q0' H				Q0 H			
Q1Q2 B S	00	01	11	10	00	01	11	10
00		1				X	X	X
01		1				X	X	X
11		1				X	X	X
10		1				X	X	X

	Q0' F				Q0 F			
Q1Q2 B S	00	01	11	10	00	01	11	10
00			1			X	X	X
01			1			X	X	X
11			1			X	X	X
10			1			X	X	X

	Q0' L				Q0 L			
Q1Q2 B S	00	01	11	10	00	01	11	10
00		1		1		X	X	X
01		1		1		X	X	X
11		1		1		X	X	X
10		1		1		X	X	X

(3 pts) List your final design equations and required logic gates (including types of Flip Flops) needed to complete this circuit.

- Equations
 - $Q_2^+ = B + Q_0'Q_1'Q_2'S$
 - $Q_1^+ = B'(Q_1 \oplus Q_2) + Q_1Q_2B + Q_1BS'$
 - $Q_0^+ = B'S'(Q_1 \oplus Q_2)'$
 - $H = Q_1'Q_2$
 - $F = Q_1Q_2$
 - $L = Q_1 \oplus Q_2$
- Logic gates
 - XOR * 1 (XOR $Q_1 \oplus Q_2$ pair is repeated, so only one pair will be used in circuit)
 - AND * 7
 - OR * 2
 - D-FLIP FLOP, ASYNCHRONOUS * 3

Task C-3: Determine Criteria and Weighting for Judging Your Designs

(5 pts) Using the guidelines in the laboratory FAQ's, list your 5 criteria and associated weights here used to help decide between the two design models (weights should add to 100%);

Commented [A2]: criteria

Criteria	Weight
Number of gates	15%
Number of flip flop	10%
Adherence to stockholder findings	45%
You're understanding to the machine	5%
Is it working?	25%

Task C-4: Apply the Criteria to Pick the Best Design

(2 pts) Describe how you applied each of the criteria and weighting system in the above task to pick the best design. How did you choose these criteria (customer interviews, engineering preference)?

Regarding my criteria choices, I picked them based on the FAQ's criteria and factors that may affect the stakeholders. For the weights, I first ranked the criteria by whether the criteria impacted the design's functionality, if the criteria would deviate greatly per design, and if the stakeholders cared about the criteria. Then I would assign weights that maintained those rankings.

(3 pts) Which design is better based on your criteria and weighting system and why? Please explain how the winning design scored in each category and why (the winning design does not need to score the highest in every category, but it does need to score higher overall when applying the criteria weights).

Commented [A3]: Design scoring

Design 2 is the better design based on my criteria.

1. Number of gates scores

a. $\text{score} = \frac{1}{1.024^{\text{total gates}}} \times 100\%$

b. Design 1 score = 82.72%

c. Design 2 score = 78.89%

2. Number of flip flop

a. $\text{Score} = \frac{1}{1.0573^{\text{total flip flops}}} \times 100\%$

b. Design 1 score = 84.61%

c. Design 2 score = 84.61%

3. Adherence to stockholder findings

a. Score

i. $\text{Score} = \frac{\text{total adhered findings}}{3} \times 100\%$

ii. Designs can partially adhere to a finding, meaning they count as 0.5 adhered finding.

b. Design 1 score = $\frac{0.5+1+0}{3} \times 100\% = 50\%$

c. Design 2 score = $\frac{1+0.5+1}{3} \times 100\% = 83\%$

4. My understanding of the machine

a. Scoring

i. Absolute = 100%

ii. Broadly = 66%

iii. Vaguely = 33%

iv. Nonexistent = 0%

b. Design 1 score = 66%

c. Design 2 score = 33%

5. Is it working?

a. Scoring

- i. Yes = 100%
- ii. Sort of = 50%
- iii. No = 0%

b. Design 1 score = 100%

c. Design 2 score = 100%


6. **Composite scores**

- a. Design 1 = $82.72\% \times 0.15 + 84.61\% \times 0.10 + 50\% \times 0.45 + 66\% \times 0.05 + 100\% \times 0.25 = 72\%$
- b. Design 2 = $78.89\% \times 0.15 + 84.61\% \times 0.10 + 83\% \times 0.45 + 33\% \times 0.05 + 100\% \times 0.25 = 84\%$

Commented [A4]: Composite

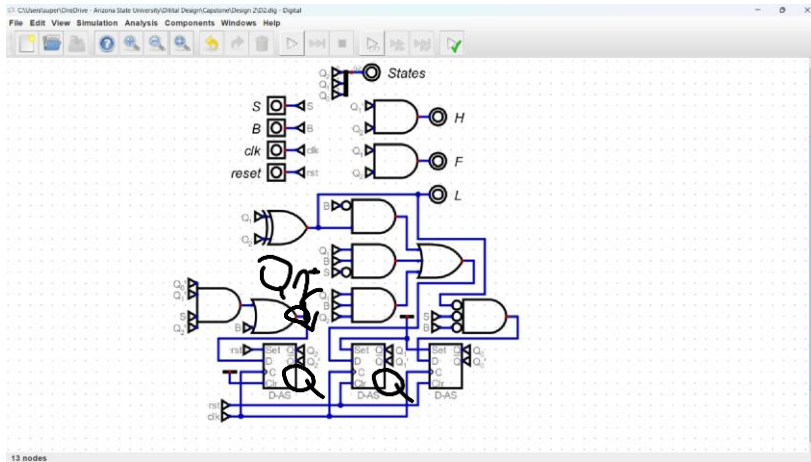Task C-5: Build and Simulate Winning Design in Digital

(15 pts) Insert a copy of your chosen Digital Schematic here. Please make sure that you have outputs or tunnels connected to each flip flop so that you can easily monitor your states. Make sure that the logic and equations match the final equations presented in either Design 1 or Design 2.



Task C-6: Record a Video Demonstration of the Winning Design

(15 pts) Record a video demonstration showing all positions being visited and various combinations of the inputs in Digital. For every clock cycle, explain the inputs, what current state you are in, and point out any outputs that should be noted. Be sure to show what happens for different input combinations at each position. That is, your demonstration should be able to showcase all possible states and transitions required to get there. If you include any asynchronous inputs, make sure to

show those features as well. Add a link to your video below. Be sure to include any required password.

Video link: https://asu.zoom.us/rec/share/vqy4Fkthjky9ioY7eDqnC_IHfGlm7Ib9fPOJnwhIU-RqCfyW1nRJZScO3xynxztA.4zciq4DOBLWW1j6Q?startTime=1713905946000

Passcode: 3lh?ee#b

Task C-7: Fill Out the Self-Assessment and Turn in Your Design

There are two items to submit. Turn in the zip file of your capstone project folder. Also turn in this template once it is filled out. There will be a deduction of 5 points if your template is only found inside the zip folder. The self-assessment is on the next page.

SELF-ASSESSMENT WORKSHEET

Put an 'X' in the table below indicating how strongly you agree or disagree that the outcomes of the assigned tasks were achieved. Use '5' to indicate that you 'strongly agree' and '1' to indicate that you 'strongly disagree'. Use 'NA', Not Applicable, when the tasks you performed did not elicit this outcome. Credit will be given for including this worksheet with your lab report. However, your **responses will not be graded**, they are for your instructor's information only.

Table 1: Self-Assessment of Outcomes for the Capstone Design Project Lab.

After completing the assigned tasks and report I am able to:	5	4	3	2	1	NA
Initiate a design process based on a value proposition and feedback from various stakeholders.			X			
Make assumptions to complete an incomplete functional specification.	X					
Use classical design techniques (i.e., state diagrams, state transition tables, and Karnaugh Maps), to design a synchronous sequential machine starting with a functional specification.	X					
Build, and debug a synchronous sequential machine.	X					
Develop reasonable engineering criteria for comparing different designs.				X		
Apply engineering criteria to select a 'best' design.	X					

Write below any suggestions you have for improving this laboratory exercise so that the stated learning outcomes are achieved.

CAPSTONE DESIGN PROJECT: LAB REPORT GRADE SHEET

Name:

Grading Criteria	Max Points	Points lost
Template		
Neatness, Clarity, and Concision	5	
Description of Assigned Tasks, Work Performed & Outcomes Met		
Task C-1: Planning the Synchronous Sequential Machines	15	
Task C-2: Document the Synchronous Sequential Machines	40	
Task C-3: Determine Criteria and Weighting for Judging Your Designs	5	
Task C-4: Apply the Criteria to Pick the Best Design	5	
Task C-5: Build and Simulate Winning Design in Digital	15	
Task C-6: Record a Video Demonstration of the Winning Design	15	
Self-Assessment Worksheet (The content of the self-assessment worksheet will not be graded. Full credit is given for including the completed worksheet.)	(2 extra points)	
Lab Score	Points Lost	
	Late Lab	
	Lab Score	